

Question	Answers	Extra information	Mark
01.1	correct symbol for voltmeter drawn		1
	voltmeter drawn in parallel to bulb		1
01.2	resistance = potential difference ÷ current	Allow correct rearrangement.	1
01.3	resistance = $\frac{12}{6}$	Allow correct use of equation from 01.2 .	1
	2 ohms/Ω	An answer of 2Ω with no working shown scores 3 marks.	1
01.4	add another cell		1
Total			7



Question	Answers	Extra information	Mark
02.1	A series (circuit)	Answers in this	1
	B parallel (circuit) order only.	order only.	1
02.2	ammeter		1
02.3	series circuit/circuit A:		
	 current is the same everywhere in the circuit potential difference is split between the components 		1
	 parallel circuit/circuit B: current is shared between the components/branches potential difference is the same across the components in each branch 		1
Total			7



Question	Answers	Extra information	Mark
03.1	electrostatic (force)		1
03.2	electrons were transferred from the student's hair to the balloon		1
	the student's hair had more protons than electrons		1
	protons are positively charged		1
03.3	the balloon is negatively charged		1
	opposite charges attract		1
Total	Total		6



Question	Answers	Extra information	Mark
04.1	Any three from:		3
	 wrap the insulated copper wire around the iron nail attach crocodile clips to each end of the insulated copper wire attach the crocodile clips to the power pack switch on the power pack to allow a current to flow through the wire 		
04.2	the paperclips are magnetic/made of a magnetic material	Allow the paperclips are made of iron/ steel.	1
04.3	correct scale on <i>y</i> -axis	Scale must take up at least half of the grid.	1
	all points plotted correctly	Allow 1 mark for 4 or 5 points plotted correctly.	2
	straight line of best fit		1
04.4	as the current increases, the strength of the electromagnet increases		1
04.5	Any one from:		1
	 the electromagnet can be switched on and off the strength of the magnetic field can be varied 		
Total			10