
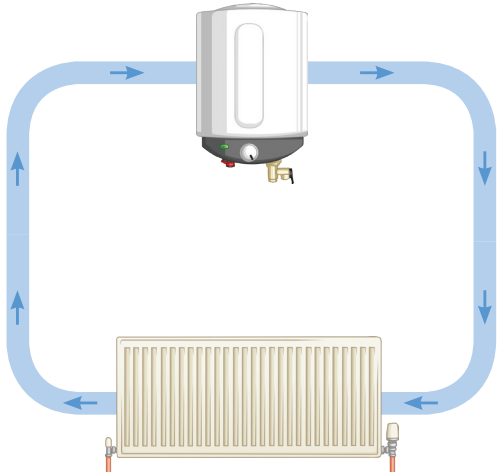


Model Evaluation Activity

Model	
<p>1.</p> 	<p>In this model, what represents the following: Keywords: charge, same, series, not, charge.</p> <p>a) current _____</p> <p>b) battery _____</p> <p>c) wires _____</p> <p>d) bulb _____</p> <p>Use this model to describe electric current in a circuit.</p> <p>Current is the flow of _____ around a circuit. The faster the _____ flows, the higher the current. The current is the _____ everywhere in a _____ circuit. Current is _____ used up.</p>
<p>2.</p> 	<p>In this model, what represents the following: If the pipes became narrower, how would this have an impact on the flow of water?</p> <p>Keywords: narrow, harder, current, resistance.</p> <p>a) current _____</p> <p>b) battery _____</p> <p>c) wires _____</p> <p>d) bulb _____</p> <p>e) switch _____</p> <p>f) voltmeter _____</p> <p>Use your model to explain how electricity flows through a circuit.</p> <p>It would be _____ for the water to travel around the system. A _____ pipe means increased _____ ; increased resistance leads to a smaller _____.</p>

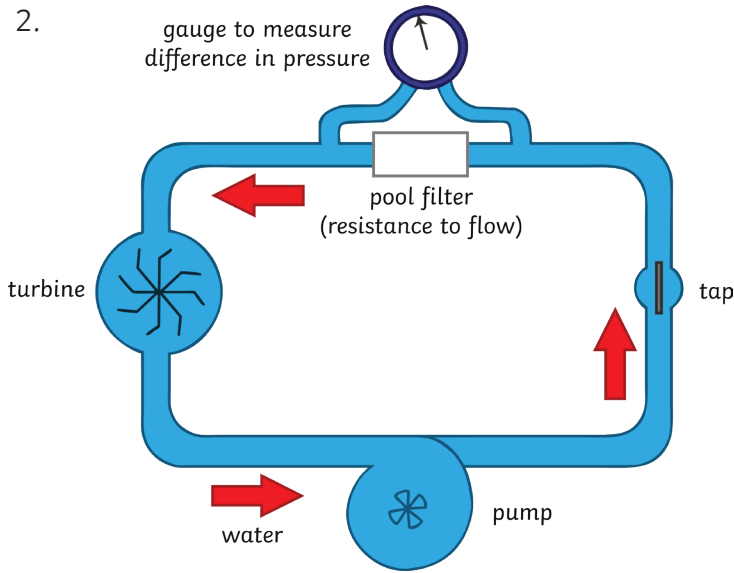

3. In the space provided, create your own model.

In this model, what represents the following:

a) current _____

b) battery _____



c) wires _____

d) bulb _____

Use your model to explain how electricity flows through a circuit.



Model Evaluation Activity Answers

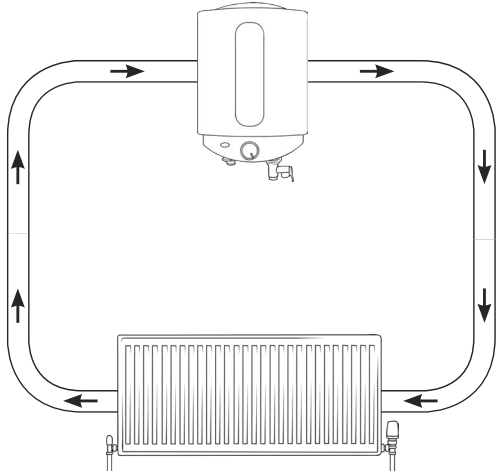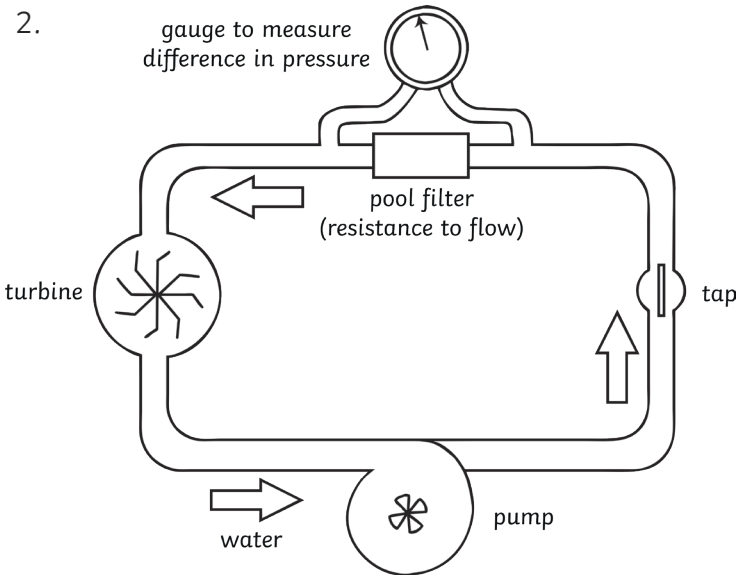Model	
<p>1.</p> 	<p>In this model, what represents the following:</p> <ul style="list-style-type: none"> a) current flow of water b) battery pump and boiler c) wires pipes d) bulb radiator <p>Use this model to explain electric current in a circuit.</p> <p>Current is the flow of charge around a circuit. The faster the charge flows, the higher the current. The current is the same everywhere in a series circuit. Current is not used up.</p>
<p>2.</p> 	<p>In this model, what represents the following:</p> <ul style="list-style-type: none"> a) current flow of water b) battery pump c) wires pipes d) bulb turbine e) switch tap f) voltmeter pressure gauge <p>Use your model to explain how electricity flows through a circuit.</p> <p>If the pipes became narrower, how would this have an impact on the flow of water?</p> <p>Keywords: narrow, harder, current, resistance.</p> <p>It would be harder for the water to travel around the system. A narrow pipe means increased resistance; increased resistance leads to a smaller current.</p>

