
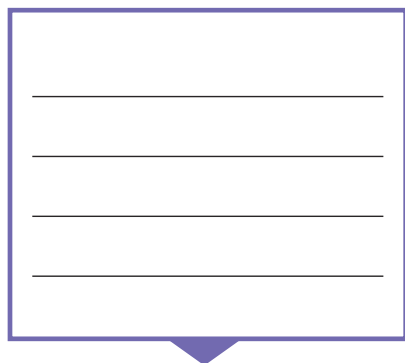


Rope Model

 
Today we have used a model to explain how electrical circuits work. Use the pictures below to help you describe what is happening at each stage of the circuit. Use the following keywords to help you: **voltage**, **current**, **battery**, **resistance**, **energy**.




Four horizontal lines for writing notes.



Four horizontal lines for writing notes.

 

Four horizontal lines for writing notes.

 

Four horizontal lines for writing notes.



Jelly Bean Model

Today we have used a model to explain how electrical circuits work. Use the pictures below to help you describe what is happening at each stage of the circuit. Use the following keywords to help you: **voltage**, **current**, **battery**, **resistance**.

