
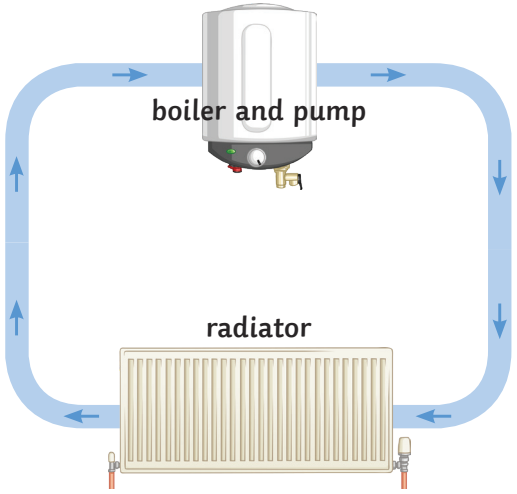


# Model Evaluation Activity

Model	
<p>1.</p> 	<p>In this model, what represents the following: Use this model to <b>explain</b> electric current in a circuit.</p> <p>a) current _____</p> <p>b) battery _____</p> <p>c) wires _____</p> <p>d) bulb _____</p> <p>Current is... _____</p> <p>_____</p> <p>_____</p> <p>_____</p>
<p>2.</p> 	<p>In this model, what represents the following: If the pipes became <b>narrower</b>, how would this have an impact on the flow of water?</p> <p>a) current _____</p> <p>b) battery _____</p> <p>c) wires _____</p> <p>d) bulb _____</p> <p>e) switch _____</p> <p>f) voltmeter _____</p> <p>If the pipes became narrower it would have an impact on the flow of water because...</p> <p>_____</p> <p>_____</p> <p>_____</p>

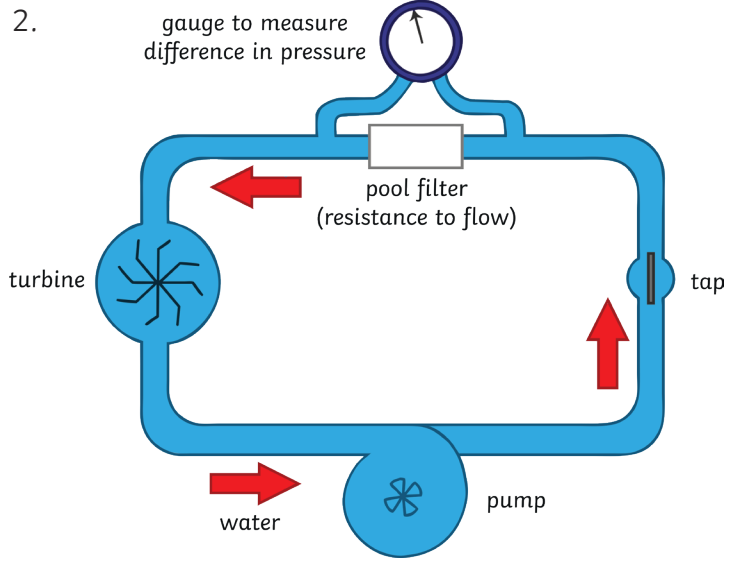

3. In the space provided, create your own model.

In this model, what represents the following:

- a) current \_\_\_\_\_
- b) battery \_\_\_\_\_
- c) wires \_\_\_\_\_
- d) bulb \_\_\_\_\_

**Describe** the strengths (good points) of the model.

The strengths of my model are... \_\_\_\_\_

---

---

**Describe** the weaknesses (bad points) of the model.

The weaknesses of my model are... \_\_\_\_\_

---

---

Use your model to explain how electricity flows through a circuit.

---



---

---

---



# Model Evaluation Activity Answers

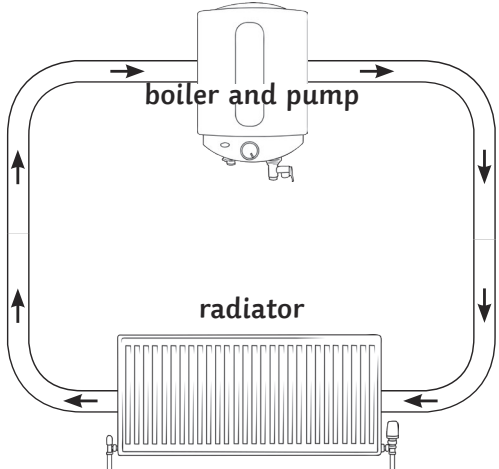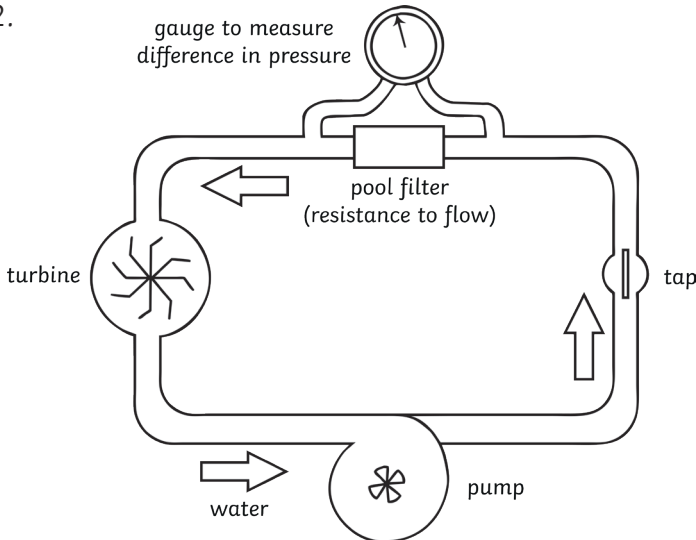Model	
<p>1.</p> 	<p>In this model, what represents the following:</p> <ul style="list-style-type: none"> <li>a) current <b>flow of water</b></li> <li>b) battery <b>pump and boiler</b></li> <li>c) wires <b>pipes</b></li> <li>d) bulb <b>radiator</b></li> </ul> <p>Use this model to <b>explain</b> electric current in a circuit.</p> <p><b>Current is the flow of charge around a circuit. The faster the charge flows, the higher the current. The current is the same everywhere in a series circuit. Current is not used up.</b></p>
<p>2.</p> 	<p>In this model, what represents the following:</p> <ul style="list-style-type: none"> <li>a) current <b>flow of water</b></li> <li>b) battery <b>pump</b></li> <li>c) wires <b>pipes</b></li> <li>d) bulb <b>turbine</b></li> <li>e) switch <b>tap</b></li> <li>f) voltmeter <b>pressure gauge</b></li> </ul> <p>If the pipes became <b>narrower</b>, how would this have an impact on the flow of water?</p> <p>If the pipes became narrower it would have an impact on the flow of water because...</p> <p><b>It would be increasingly difficult for the water to travel around the system. A narrow pipe means increased resistance; increased resistance leads to a smaller current.</b></p>

